

III- SEM -ELEC/ ELEC(PT)/E&EE/E&ME(IC)/2019(W)/(New)

Th. 2 - CIRCUIT & NETWORK THEORY

Full Marks: 80

Time : 3 Hours

Answer any FIVE Questions including Q No. 1& 2

Figures in the right hand margin indicates marks

1. Answer ALL the Questions: [2x10]
- (a) Define Retentivity ?
 - (b) What do you mean by Coefficient of Coupling ?
 - (c) Draw the power triangle and derive the formula for apparent power?
 - (d) State Superposition Theorem.
 - (e) What is Bilateral element ? Give at least two examples?
 - (f) Define Quality Factor.
 - (g) Define Filter in electrical circuit
 - (h) What is power factor?
 - (i) State Blondel's Theorem.
 - (j) Find the current across 5Ω resistor in the circuit as shown in Figure 1.

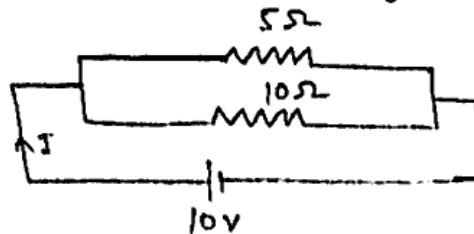


Figure 1

2. Answer any SIX questions: [5x6]
- (a) Explain Briefly the 3ph power measurement by 2-Wattmeter method for Star connection load only?
 - (b) Find the total inductance of the three series connected coupled coil as shown in the Figure 2.

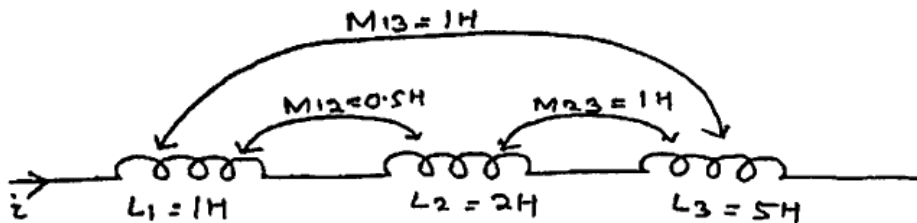


Figure 2

- (c) State and Explain Maximum Power Transfer Theorem.
- (d) Find the current in series R-L circuit having $R = 2\Omega$ AND $L = 10\text{ H}$ while D.C voltage of 100V is applied. What is the value of this current after 5sec of switching on ?
- (e) Derive the Relation between Line and Phase quantities in STAR connection?
- (f) In series RLC circuit has $R = 2\Omega$, $L = 2\text{ mH}$ and $C = 10\mu\text{F}$. Calculate (i) Q- Factor of the circuit (ii) Bandwidth (iii) The Resonant frequency (iv) the half power frequency f_1 and f_2 .
- (g) The unbalanced Bridge circuit is shown in Figure 3. Find the value of current in $R_1 = 50\Omega$

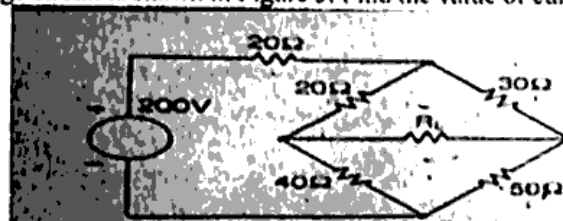


Figure 3

3. Consider the Figure 4 as shown below. Find the voltage at different node by using SUPERNODE analysis? [10]

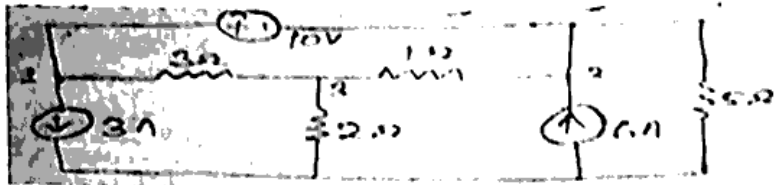


Figure 4

4. Explain Briefly Hysteresis loop in a ferromagnetic material? [10]
5. Obtain the open circuit parameter (Z-Parameter) and loop quantities of the network shown in Figure 5. [10]

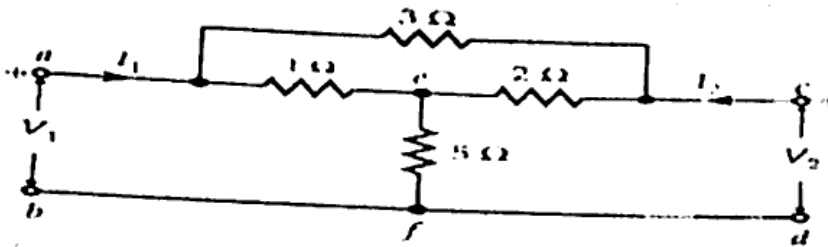


Figure 5

6. Find the current in the 3Ω resistor for the circuit as shown in Figure 6 by using Thevenin Theorem. [10]

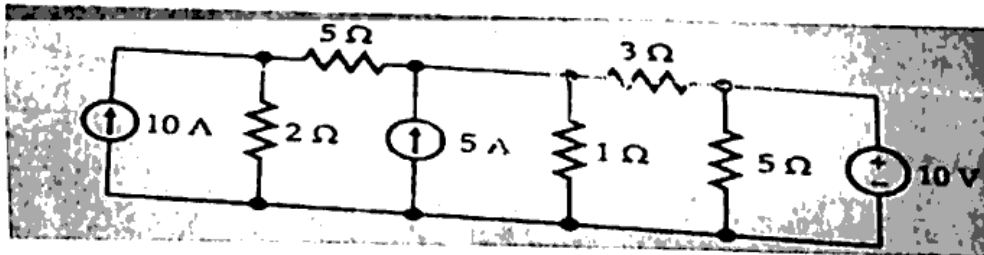


Figure 6

7. Design a Prototype Band Pass Filter to match with a load of 600Ω and allow frequencies between 3KHZ and 6KHZ. [10]