

BASIC ELECTRONICS ENGG.

(Theory – 4(b))

Full Marks : 40

Time : $1\frac{1}{2}$ hours

Answer any four questions including Q. Nos. 1 & 2

Figures in the right-hand margin indicate marks

1. Answer *all* the questions : 2 × 5
- (a) What is PIV ?
 - (b) Define Ripple factor. What is its value for half wave rectifier ?
 - (c) What is demodulation ?
 - (d) What is electron emission ? Name the types of the emission.
 - (e) Define transistor biasing. What is the need of biasing ?
2. Answer any *three* : <http://www.sctevtonline.com> 5 × 3
- (a) Explain the operation of full wave rectifier with its advantages and disadvantages.
 - (b) With proper diagram describe the operation of capacitor input filter.
 - (c) Write down the difference between intrinsic and extrinsic semiconductor.
 - (d) Discuss different types of modulation with proper waveforms.
3. What is multimeter ? Explain the multimeter as ammeter, voltmeter and ohmmeter. $7\frac{1}{2}$
4. With proper block diagram, explain the function of each block of CRO. $7\frac{1}{2}$
5. (a) Explain the operation of LED with its advantages. $3\frac{1}{2}$
- (b) Classify solid according to electrical conductivity with respect to energy band diagram. 4